

① Gauss's Law Problems\* For static charge distributions

$$\oint \vec{E} \cdot d\vec{A} = \frac{q_{enc}}{\epsilon_0}$$


allows us to compute  $\vec{E}$  and

$$\text{also } V(b) - V(a) = -\int_a^b \vec{E} \cdot d\vec{r}$$

\* Three variations



spheres and spherical shells

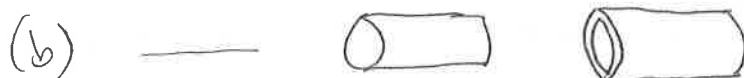Lines, cylinders,  
cylindrical shells

Plates

\* Usually left-hand side of Gauss's Law is easiest part of calculation. For the three geometries above

(a)  $E(4\pi r^2)$  Gaussian sphere with radius  $r$ (b)  $E(2\pi r L)$  Gaussian cylinder with radius  $r$  and length  $L$ (c)  $E(A)$  Gaussian "cylinder" with face area  $A$

\* Right-hand side of Gauss's Law can be more challenging.

(i) For "uniform" charge distributions  $\rho = \frac{Q_{\text{total}}}{V_{\text{total}}}$  and

$$q_{\text{enc}} = \rho \cdot \text{Volume}_{\text{enc}}$$

(ii) For "nonuniform" charge distributions  $\rho(r)$ :

$$dq_{\text{enc}} = \rho(r) dV$$

$$\Rightarrow q_{\text{enc}} = \int \rho(r) dV$$

(a) Spherical Gaussian surfaces  $dV = 4\pi r^2 dr$

(b) Cylindrical Gaussian surfaces  $dV = 2\pi r L dr$


\* Once  $\vec{E}$  field is known everywhere, it is possible to compute the potential difference  $\Delta V = V(b) - V(a)$   
 $= - \int_a^b \vec{E} \cdot d\vec{r}$  between any two points in space.

\* Can also compute capacitance  $C = \frac{Q}{\Delta V}$ , where


$\Delta V$  is the potential difference between the two conductors and  $Q$  is the magnitude of the charge on the conductors.

② Ohm's Law

\* Crucial point is that current  $i$  is constant along the direction of flow but current density  $j = \frac{i}{A}$  can vary.   
 ← cross sectional area  $A$ .

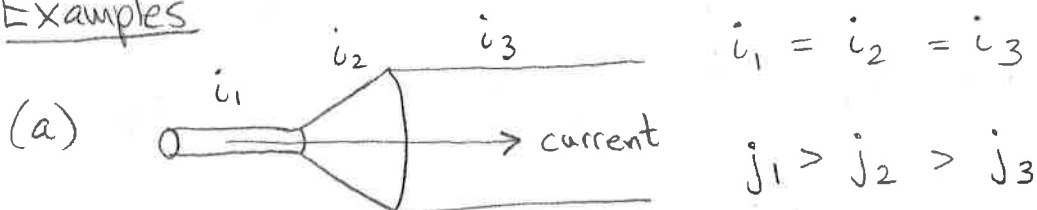\* Examples

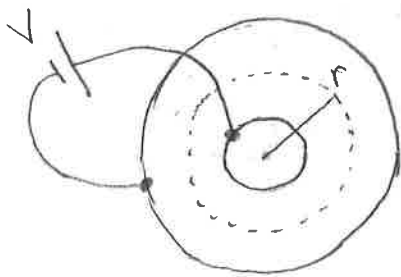
(b) Spherical shell with current flowing from inner surface to outer surface



$i = \text{constant}$  through shell of radius  $r$   
 $j$  is decreasing for larger  $r$ :


$$j = \frac{i}{4\pi r^2}$$

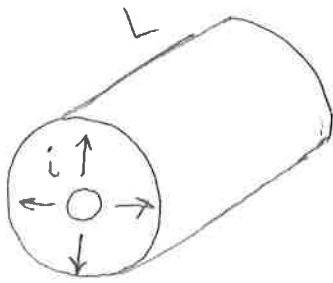(c) For cylindrical shells, current can flow either from inner to outer surface or along the length of the cylinder depending on how we connect the battery



$$\text{Here } j = \frac{i}{2\pi r L}$$

(decreases as  $r$  increases)

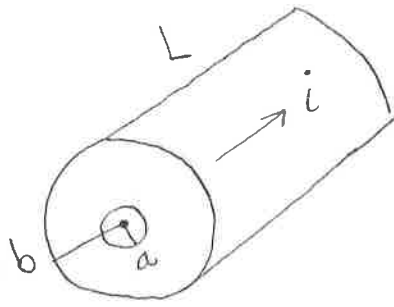

$$\text{Here } j = \frac{i}{\pi(b^2 - a^2)}$$

\* To calculate the resistance of an object, the current, the current density, or  $\vec{E}$  field, follow these 5 steps:

(1) Identify current direction, and label current "i"

(2) Find cross sectional area  $A$  perpendicular to current flow and calculate current density  $J = \frac{i}{A}$ .

(3) Find electric field from Ohm's Law:  $E = \rho J$  resistivity

(4) Compute  $\Delta V = -\int \vec{E} \cdot d\vec{r} = -\int \rho J dr$


In general either  $\rho$  or  $J$  can vary along the direction of the current:  $\Delta V = -\int \rho(r) J(r) dr$

(5) Obtain  $R$  from Gauss's Law:  $\Delta V = iR$

\* Resistors in  $\left\{ \begin{array}{l} \text{parallel} \\ \text{series} \end{array} \right. \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $R_{eq} = R_1 + R_2$

③ Circuits

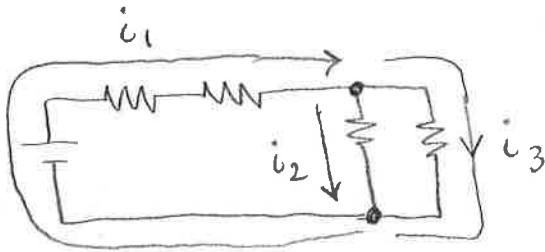\* Current  $i$  is constant along any continuous section of the circuit and only changes at a junction




\* Always analyze circuits in the following steps

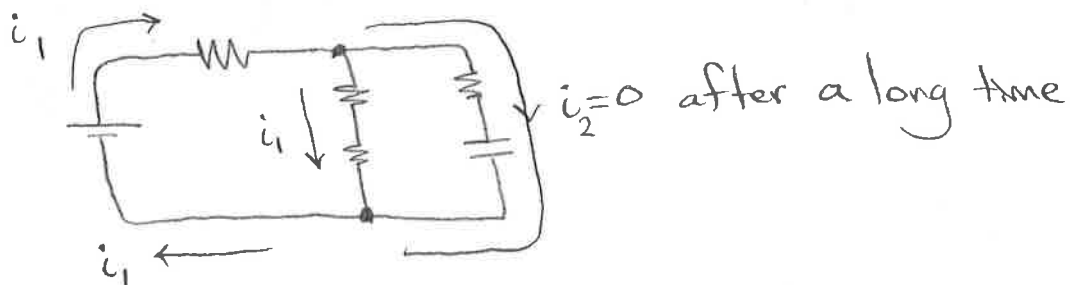a) Draw one current for each section of wire and label both the magnitudes ( $i_1, i_2, i_3, \dots$ ) and directions.


Note: choice of current direction doesn't matter

Note: If there is a capacitor in a section of wire, then after a long time charge will build up and current flow stops through the entire section



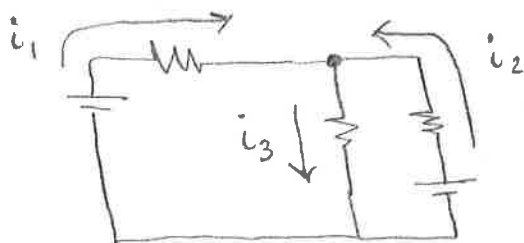
(b) At a junction, write down equation for current conservation:

$$i_{in} = i_{out} \quad (\text{here choice of current direction factors in})$$



$$i_1 + i_2 = i_3$$

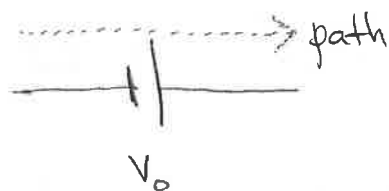
(c) Use the loop rule ( $\Delta V = 0$  around closed path) as many times as needed to generate  $N$  equations for  $N$  unknowns. Calculate individual potential gains/drops across circuit elements as follows:



$+V_0$  from  $-$  to  $+$  terminal

$-V_0$  from  $+$  to  $-$  terminal

(independent of current direction)

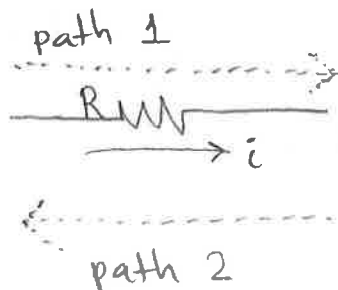


$\Delta V = -iR$  for path 1 (in direction of current)

$\Delta V = +iR$  for path 2 (where path is opposite direction of current)



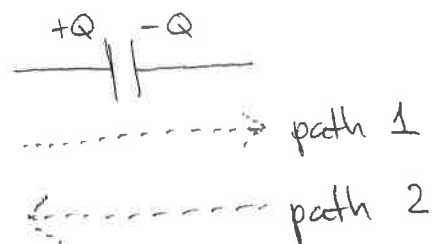$\Delta V = 0$  if current is 0 (for instance if there is a capacitor in series)




$$\Delta V = -\frac{Q}{C} \quad (\text{for path 1 from } + \text{ to } -)$$

$$\Delta V = +\frac{Q}{C} \quad (\text{for path 2 from } - \text{ to } +)$$

⊛ Note that your choice of path is completely independent from the current direction (you can walk with or against the current in taking a closed path)

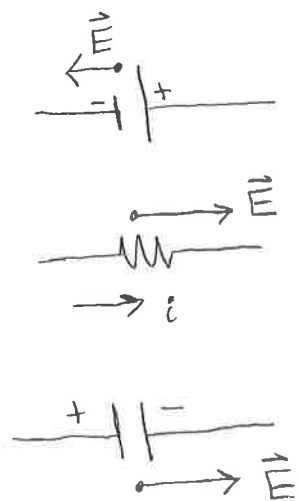⊛ If you are ever unsure about the sign on a potential drop/gain, think about the direction of the electric field



Moving with  $\vec{E}$  field results in potential drop (-).

Moving against  $\vec{E}$  field results in potential gain (+).