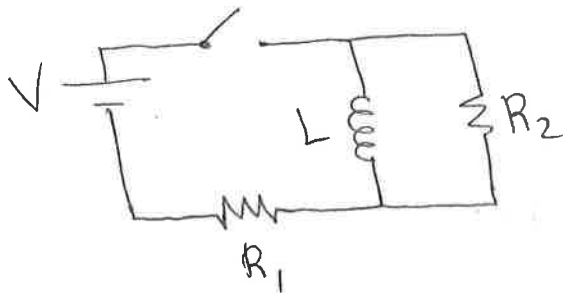


Example (Exam 3, 2011, Q3)



When switch is closed for long time, no current flows through R_2 since inductor provides no pushback $(-L \frac{di}{dt})$ to current flow.


Current through R_1 :

$$V - L \frac{di}{dt} - iR_1 = 0$$

$$i = \frac{V}{R_1}$$

Now open switch. Current i cannot change discontinuously through inductor $\Rightarrow i(0) = \frac{V}{R_1}$.

New Kirchhoff loop rule

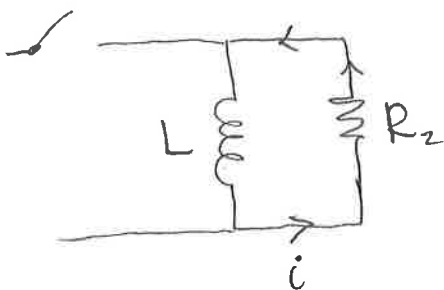

$$-L \frac{di}{dt} - iR_2 = 0$$

$$L \frac{di}{dt} = -iR_2$$

$$\frac{di}{i} = -\frac{R_2}{L} dt$$

$$\int_{i(0)}^{i(t)} \frac{di}{i} = -\frac{R_2}{L} \int_0^t dt$$

$$\left[\ln i \right]_{i(0)=V/R_1}^{i(t)} = -\frac{R_2}{L} t$$

$$\ln(i(t)) - \ln(V/R_1) = -\frac{R_2}{L} t$$

$$\ln\left(\frac{R_1}{V} i(t)\right) = -\frac{R_2}{L} t$$

$$\frac{R_1}{V} i(t) = e^{-\frac{R_2}{L} t}$$

$$i(t) = \frac{V}{R_1} e^{-\frac{R_2}{L} t}$$